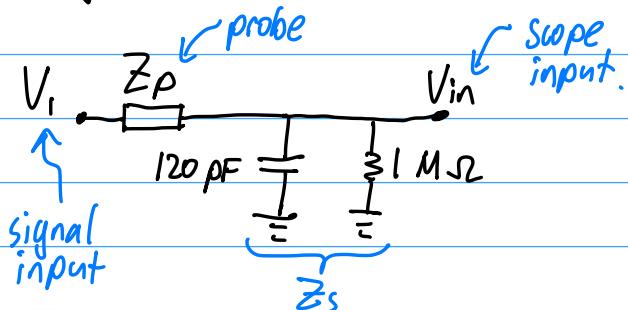


## AoE Ex 1.44

Design a 10x oscilloscope probe.



$$V_{in} = \frac{V_1 Z_s}{Z_s + Z_p}$$

$$\text{where } Z_s = 1 \text{ M}\Omega \parallel 120 \text{ pF}.$$

Require  $20 \text{ dB} = 10^{\frac{20}{20}} = 10$  times attenuation.

$$\therefore \frac{V_{in}}{V_1} = \frac{1}{10} = \frac{Z_s}{Z_s + Z_p}$$

$$Z_s + Z_p = 10 Z_s$$

$$Z_p = 9 Z_s$$

Need to select a network where  $Z_p = 9 Z_s$  at all frequencies. Propose  $Z_p = \frac{1}{C_p R_p}$  for some  $R_p$  &  $C_p$ .

To make a parallel combination larger by 9, increase both impedances by 9.

$$\left[ \text{Proof: } 9 Z_1 \parallel 9 Z_2 = \frac{9 Z_1 \times 9 Z_2}{9 Z_1 + 9 Z_2} = \frac{9^2 Z_1 Z_2}{9(Z_1 + Z_2)} = 9 (Z_1 \parallel Z_2) \right]$$

$\therefore R_p = 9 \text{ M}\Omega$ . smaller C  $\Rightarrow$  larger impedance.

$$C_p = \frac{120}{9} \text{ pF} = 13.3 \text{ pF}$$

The 10x probe is:

