## AOE Ex 2.1

3.3 V

LED V. L. SV

LED V. L. SV

Guess LED drops  $\approx$  1.8 V

330  $\Omega$  as per Fig 2.8.

Vin 10 h.r.  $\Omega_{\rm c}$  +  $\Omega_{\rm c}$  2 N3404 datasheet shows

The 2 N3404 datasheet shows

Typ. VcE in Saturation  $\approx$  0.1 V. What is the LED current? Min B?

Considering these voltages,  $I_1 = \frac{3.3-1.8-0.1}{330} = 4.2 \text{ mA}.$ 

Also  $I_B \approx \frac{3.3 - 0.7}{10000} = 0.26 \text{ mA}.$ Required  $\beta = \frac{4.2 \text{ mA}}{0.26 \text{ mA}} = 16.$