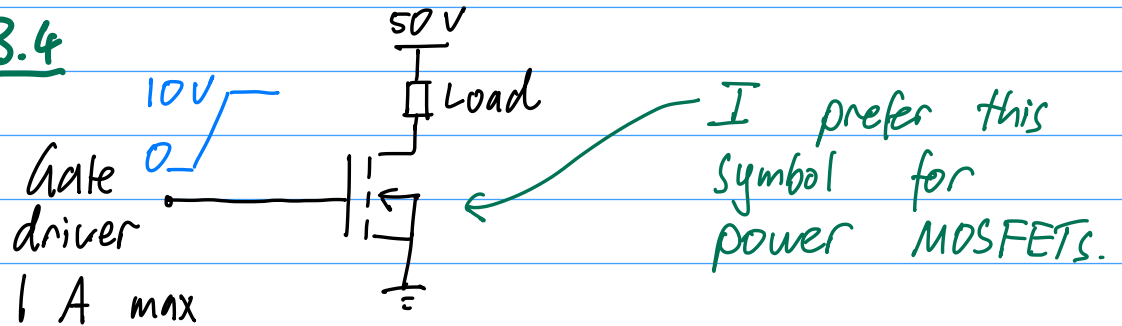


## AOE 3.4



- (a) Find switching time when treating the gate as a  $200 \text{ pF}$  load.

$$I_c = C \frac{dV}{dt} \approx C \frac{\Delta V}{\Delta t}$$

$$\Delta t = \frac{C \Delta V}{I_c}$$

Let  $I_c = 1 \text{ A}$ ,  $\Delta V = 10 \text{ V}$ ,  $C = 200 \text{ pF}$ .  
 $\Delta t = 2 \text{ ns}$ .

- (b) Find switching time to deliver  $Q_g = 40 \text{ nC}$ .

$$I = \frac{\Delta Q}{\Delta t}$$

$$\therefore \Delta t = \frac{\Delta Q}{I} = \frac{40 \text{ nC}}{1 \text{ A}} = 40 \text{ ns}$$

Even a  $1 \text{ A}$  drive current isn't enough to reach the claimed  $\approx 25 \text{ ns}$  capability of the device.