

$$(a) A_v = \frac{R_L}{R_L + \frac{1}{g_m}}$$

$$R_L + \frac{1}{g_m} = \frac{R_L}{A_v}$$

$$\frac{1}{g_m} = \left(\frac{1}{A_v} - 1\right) R_L$$

$$= \left(\frac{1}{0.9} - 1\right) 8$$

$$= 0.889 \Omega$$

$$g_m = 1.125 \text{ S.}$$

$$\therefore I_c = g_m V_T = 1.125 \times 0.026 = 29.25 \text{ mA.}$$

$$(b) \text{ By KCL, } I_L = I_c - I_1$$

$$\text{By KVL, } V_{cc} = V_{CE} + V_{out}$$

$$= V_{CE} + (I_c - I_1) R_L$$

$$\therefore I_c = I_1 + \frac{V_{cc} - V_{CE}}{R_L}$$


The Q point is when  $V_{out} = 0$ .

$$\therefore I_{LQ} = 0 \quad \therefore I_{cQ} = I_1$$

$$\therefore \text{At the Q point: } I_1 = I_1 + \frac{V_{cc}}{R_L} - \frac{V_{CEQ}}{R_L}$$

$$\therefore V_{CEQ} = V_{cc}$$

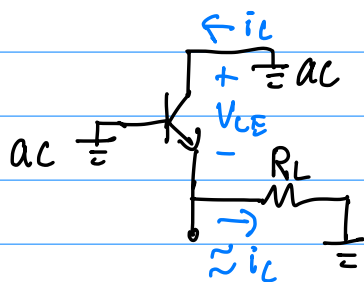(c) The AC model (with independent sources off) is:



Assume  $i_c = i_e$ .

$$\text{By KVL, } 0 = V_{ce} + i_c R_L$$

$$\text{Subst. } V_{ce} = \Delta V_{ce} = V_{ce} - V_{ceQ}$$

$$i_c = \Delta I_c = I_c - I_{cQ}$$

$$\therefore 0 = V_{CE} - V_{CEQ} + (I_C - I_{CQ}) R_L$$

Subst  $V_{CEQ} = V_{CC}$  &  $I_{CQ} = I_1$

$$0 = V_{CE} - V_{CC} + (I_C - I_1) R_L$$

$$I_C = I_1 + \frac{V_{CC}}{R_L} - \frac{V_{CE}}{R_L}$$


(d) Find the axis intercepts. Set  $I_C = 0$  first.

$$0 = I_1 + \frac{V_{CC}}{R_L} - \frac{V_{CE}}{R_L}$$

$$\begin{aligned} V_{CE(\max)} &= V_{CC} + R_L I_1 \\ &= 5 + 8 \times 29.25 \times 10^{-3} \\ &= 5.23 \text{ V.} \end{aligned}$$


Next set  $V_{CE} = 0$ .
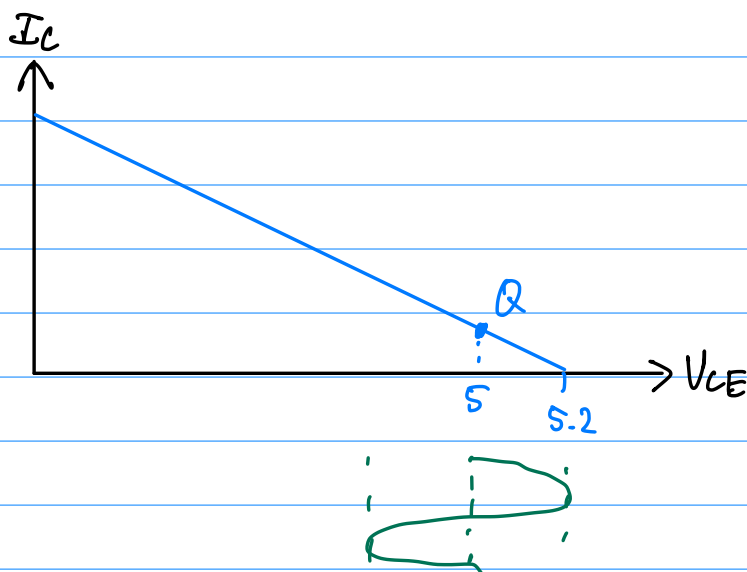
$$\begin{aligned} I_{C(\max)} &= I_1 + \frac{V_{CC}}{R_L} \\ &= 29.25 \times 10^{-3} + \frac{5}{8} \\ &= 0.65 \text{ A} \end{aligned}$$




Peak swing = 0.2 V. Peak to peak = 0.4 V.

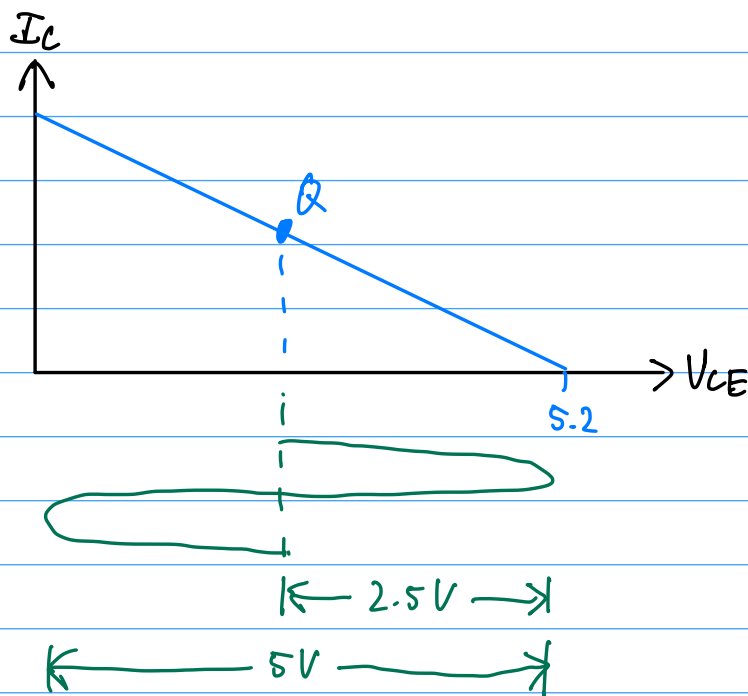(e) You may be tempted to move the Q point:



However, this would mean that  $V_{out}$  is no longer centered on 0 V.

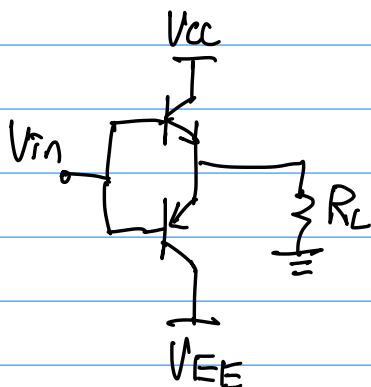Notice that this circuit has great headroom in one direction only. We can push current into  $R_L$  but can't pull it from  $R_L$ . We need another transistor. Actually  $I_1$  is a transistor anyway, so let's make it more useful.



This is a push-pull stage (class B). Hopefully you see the reasoning that leads to this design.