(a) <u>Source</u> "load"  $R_1 \lesssim \overline{V_{n_1}^2} \simeq 4kTR_1 (4)$  $\frac{R_2}{4V_{n2}^2} = 4kTR_2$ One source at  $\frac{1}{\sqrt{V_{n2}^2}} = 4kTR_2$ Of indep. sources. By superposition, consider power delivered by Uni. Next consider  $V_{nz}^2$ .  $I_{nz} = V_{nz}$  $R_1 + R_2$  $\begin{cases} R_{1} & \overline{I_{n2}^{2}} \\ \hline I_{n2} \\ \hline V_{n2} \\ \hline \end{array} & \stackrel{!}{\longrightarrow} \overline{I_{n2}^{2}} \\ \hline (R_{1} + R_{2})^{2} \\ \hline (R_{1} + R_{2})^{2} \\ \hline (R_{1} + R_{2})^{2} \\ \hline \end{array}$ Expected value  $\longrightarrow P_{RI} = \overline{I_{n2}^{2}} R_{I}$ of power delivered to  $= \frac{4kTR_1R_2}{(R_1 + R_2)^2}$ Since  $P_{P_1} = P_{R_2}$  there is no net flow of power. ... We did not break physics!

(b) 
$$R_{1}$$
 yout  
 $V_{n}^{2}$   $R_{2} = R_{1}$  Maximum power frampler  
regarizes  $R_{1} = R_{2}$ .  
 $R_{2} = R_{2}$   $V_{n} = R_{1}$   $V_{n} = V_{n}$   
 $R_{1} + R_{2}$   $R_{1} + R_{1}$   $L_{2}$   
 $V_{0ut} = \frac{R_{2}}{R_{1} + R_{2}} = \frac{4 k T R_{1}}{R_{1} + R_{1}} = k T R_{1}$ .  
 $P = \frac{V^{2}}{R}$   $P = \frac{V_{n}^{2}}{4} = \frac{4 k T R_{1}}{R_{1}} = k T$ .  
 $R = \frac{V^{2}}{R}$   $R_{1} = \frac{V^{2}}{R_{2}}$   
Think about the units.  $\left[\frac{V_{n}^{2}}{R_{1}}\right] = \frac{V^{2}}{H_{2}}$ .  
Check:  $\left[kT\right] = J$   $K = J = J \cdot S = W \cdot S = W$ .  
 $K = \frac{S}{S} = \frac{W \cdot S}{H_{2}}$   
(c).  $Bw = 1$   $GH_{2}$   $\therefore$   $P = kT \times 1 \times 10^{9}$   
 $= 1.38 \times 10^{-33} \times 300 \times 1 \times 10^{9}$   
 $= 4.14 \times 10^{-12} W$ .  
 $\therefore$  4 pW (regniting cooling to 0 K) is  
 $Rot practical J$