



No oscillation. Reasons:

1. One pole \Rightarrow not enough phase shift.

2. The circuit as drawn has $V_i = V_o$
but also $V_o = -g_m R_D V_i$

$$\therefore V_o = -g_m R_D V_o.$$

The only solution is $V_o = 0$.