



Since C_E is large,
 $V_E \approx$ ac ground
 \therefore Amp. is a basic CE stage in AC analysis.
 $\therefore V_o = V_{test} K \times (-g_m R_c)$

Loop gain = $-\frac{V_o}{V_{test}}$

$T = g_m R_c K$

(a) Set $T(j\omega) = -1$ using K from the question.

$$g_m R_c \frac{(j\omega RC)^3}{(j\omega RC)^3 + 6(j\omega RC)^2 + 5j\omega RC + 1} = -1$$

Cross-multiply & simplify $j^2 = -1$.

$$-j g_m R_c \omega^3 R^3 C^3 = -(-j\omega^3 R^3 C^3 - 6\omega^2 R^2 C^2 + 5j\omega RC + 1)$$

$$= j\omega^3 R^3 C^3 + 6\omega^2 R^2 C^2 - 5j\omega RC - 1.$$

Take real parts.

$$0 = 6\omega^2 R^2 C^2 - 1$$

$$\omega^2 = \frac{1}{6 R^2 C^2}$$

$$\therefore \omega = \frac{1}{\sqrt{6} RC} \quad \therefore f_{occ} = \frac{1}{2\pi\sqrt{6} RC}$$

(b) Take imag. parts from the equation above.

$$-g_m R_c \omega^3 R^3 C^3 = \omega^3 R^3 C^3 - 5\omega RC$$
$$0 = (1 + g_m R_c) \omega^3 R^3 C^3 - 5\omega RC$$

$$\text{Subst } \omega = \frac{1}{\sqrt{6} RC}$$

$$0 = (1 + g_m R_c) \left(\frac{1}{\sqrt{6} RC} \right)^3 R^3 C^3 - 5 \left(\frac{1}{\sqrt{6} RC} \right) RC$$

$$= \frac{(1 + g_m R_c)}{6\sqrt{6}} - \frac{5}{\sqrt{6}}$$

$$= 1 + g_m R_c - 30$$

$$g_m R_c = 29.$$

\therefore Min g_m is $\frac{29}{R_c}$.