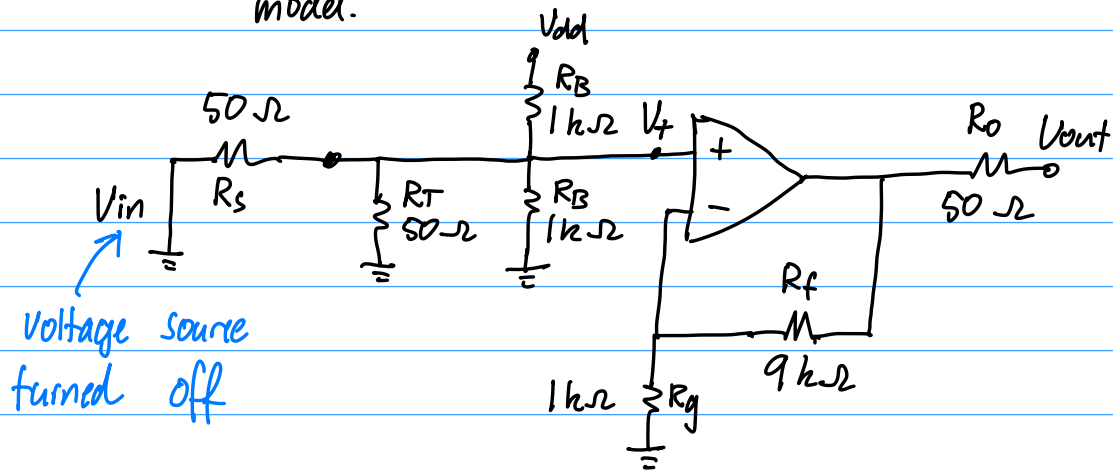


(a) Turn off V_{in} and draw the AC small signal model.




$$V_+ = \frac{(R_B \parallel R_T \parallel R_S) V_{dd}}{R_B + (R_B \parallel R_T \parallel R_S)} = 0.02381 V_{dd}.$$

$$V_{out} = \left(1 + \frac{R_f}{R_g}\right) V_+ = 10 V_+ = 0.2381 V_{dd}.$$

$$\therefore \text{Isolation} = 20 \log_{10}(0.2381) = -12.5 \text{ dB}$$

Not very much isolation.

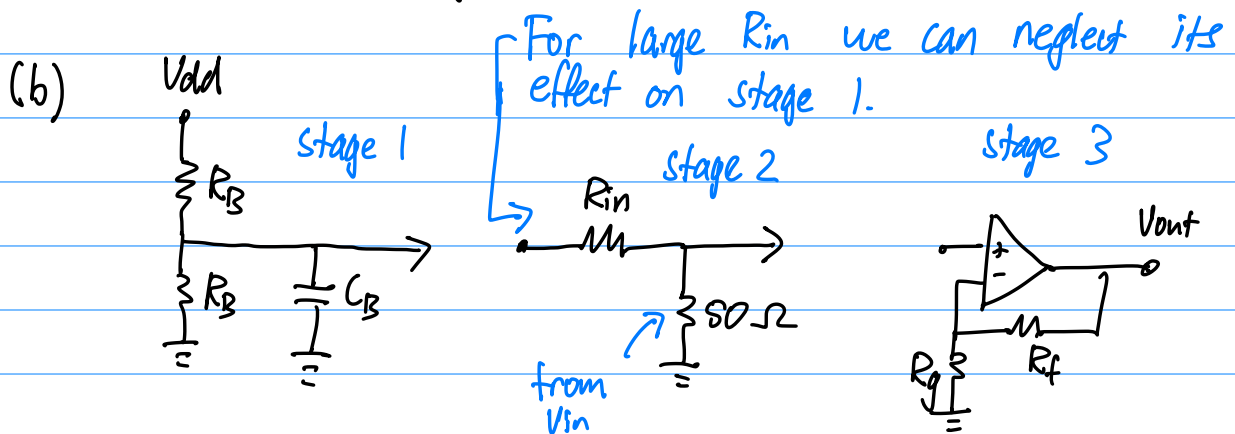

Low freq $A_v = \frac{1}{2}$
 Pole at $\omega = \frac{1}{R_B C_B / 2}$

$$A_v = \frac{50}{50 + R_{in}}$$

$$A_v = 10$$

$$\therefore \text{Low freq isolation} = \frac{1}{2} \times \frac{50}{50 + R_{in}} \times 10$$

$$= \frac{250}{50 + R_{in}}$$

Require better than -50 dB, i.e.

$$10^{-50/20} > \frac{250}{50 + R_{in}}$$

$$50 + R_{in} > \frac{250}{10^{-50/20}}$$

$$R_{in} > 79 \text{ k}\Omega$$

$$= -50.3 \text{ dB}$$

A standard value is $R_{in} = 82 \text{ k}\Omega$. ✓

$$\therefore \text{Low freq isolation} = \frac{250}{50 + 82000} = 3.047 \times 10^{-3}$$

Given the pole location $\omega = (R_B C_B / 2)^{-1}$, the transfer function is:

$$H(s) = \frac{3.047 \times 10^{-3}}{1 + R_B C_B s / 2}$$

Require $|H(j\omega)| < -100$ dB at $\omega = 2\pi \times 100 \times 10^6$

$$\therefore \left| \frac{3.047 \times 10^{-3}}{1 + R_B C_B j 2\pi \times 100 \times 10^6 / 2} \right| < \frac{-100/20}{10}$$

$$304.7 < |1 + j R_B C_B \pi \times 100 \times 10^6|$$

$$(304.7)^2 < 1^2 + 9.8696 \times 10^{16} \times R_B^2 C_B^2$$

$$9.4068 \times 10^{-13} < R_B^2 C_B^2$$

$$9.7 \times 10^{-7} < R_B C_B$$

Since we assumed $R_B/2 \ll R_{in}$ choose $\frac{R_B}{2} \approx 0.1 R_{in}$

$\therefore R_B \approx 16 \text{ k}\Omega$. Choose standard value $R_B = 18 \text{ k}\Omega$.

$\therefore C_B > 54 \text{ pF}$, Choose $C_B = 56 \text{ pF}$.

