
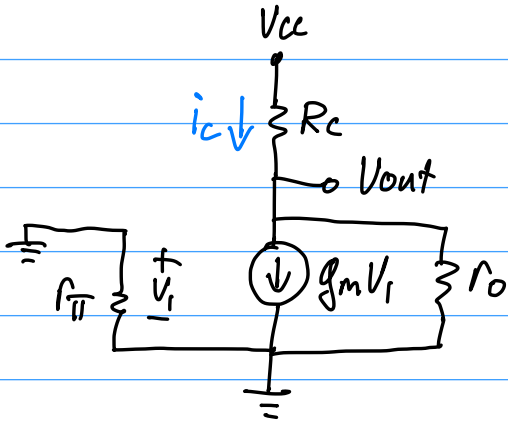


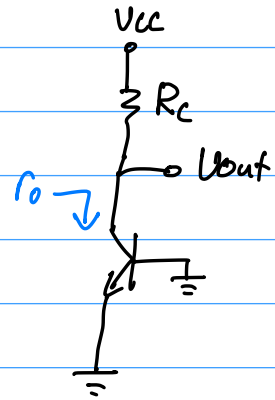10.3 (a) If the "input" is V_{CC} then V_{in} is an independent source, so is turned off ($V_{in} = 0$).



or simply




$\therefore \frac{V_{out}}{V_{CC}} = \frac{r_o}{R_c + r_o}$ by voltage divider formula.

Could also subst $r_o = \frac{V_A}{I_C}$ to obtain

$$\frac{V_{out}}{V_{CC}} = \frac{V_A}{R_C I_{EE} + V_A}$$

(b)

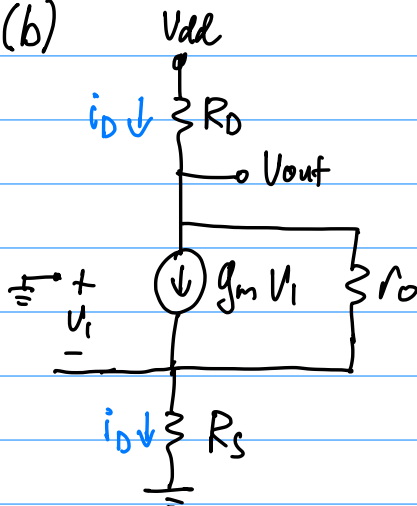

KCL at the source:

$$\frac{(-V_i)}{R_s} + \frac{(-V_i) - V_{out}}{r_o} = g_m V_i$$

$$\frac{-V_{out}}{r_o} = g_m V_i + \frac{V_i}{R_s} + \frac{V_i}{r_o}$$

$$V_i = \frac{-V_{out}}{r_o \left(g_m + \frac{1}{R_s} + \frac{1}{r_o} \right)}$$


$$i_o = \frac{(-V_i)}{R_s} = \frac{V_{out}}{g_m r_o R_s + r_o + R_s}$$

$$V_{out} = V_{DD} - i_o R_D = V_{DD} - \frac{V_{out} R_D}{g_m r_o R_s + r_o + R_s}$$

$$V_{out} + \frac{V_{out} R_D}{g_m r_o R_S + r_o + R_S} = V_{dd}$$

$$V_{out} \left(\frac{g_m r_o R_S + r_o + R_S + R_D}{g_m r_o R_S + r_o + R_S} \right) = V_{dd}$$
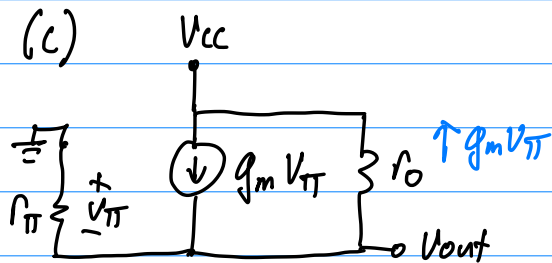
$$\frac{V_{out}}{V_{dd}} = \frac{g_m r_o R_S + r_o + R_S}{g_m r_o R_S + r_o + R_S + R_D}$$



KCL at V_{out} :

$$\frac{V_{out}}{r_{\pi}} + \frac{V_{out} - V_{cc}}{r_o} = g_m v_{\pi}$$


Notice $v_{\pi} = -V_{out}$

$$\therefore \frac{V_{out}}{r_{\pi}} + \frac{V_{out}}{r_o} - \frac{V_{cc}}{r_o} = -g_m V_{out}$$

$$(r_o + r_{\pi} + g_m r_o r_{\pi}) V_{out} = V_{cc} r_{\pi}$$

$$\frac{V_{out}}{V_{cc}} = \frac{r_{\pi}}{r_o + r_{\pi} + g_m r_o r_{\pi}} = \frac{r_{\pi}}{r_o + r_{\pi} + \beta r_o}$$

$$\because r_{\pi} = \frac{\beta}{g_m}$$

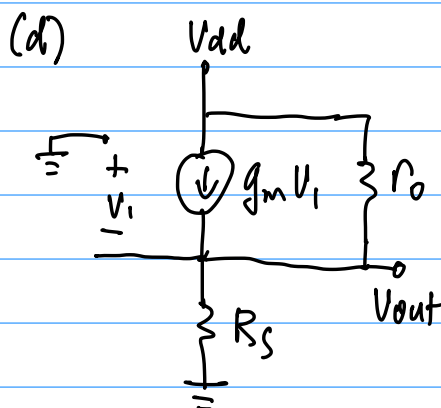

$v_i = -V_{out}$. Write KCL:

$$\frac{V_{out}}{R_S} + \frac{V_{out} - V_{dd}}{r_o} = -g_m V_{out}$$

$$(r_o + R_S + g_m r_o R_S) V_{out} = V_{dd} R_S$$

$$\frac{V_{out}}{V_{dd}} = \frac{R_S}{r_o + R_S + g_m r_o R_S}$$