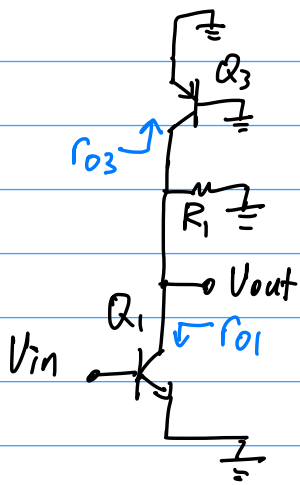


10.30 Use symmetry to find the half circuit.



$$R_{out} = R_1 \parallel r_{01} \parallel r_{03}$$

$$A_v = -g_m R_{out}$$

$$r_{01} = \frac{V_{A1n}}{I_{CQ}} = \frac{5}{0.002/2} = 5000 \Omega$$

$$r_{03} = \frac{V_{A1p}}{I_{CQ}} = \frac{4}{0.002/2} = 4000 \Omega$$

$$g_m = \frac{I_{CQ}}{V_T} = \frac{0.001}{0.026} = \frac{1}{26} \text{ S}$$

$$\therefore A_v = 50 = \frac{1}{26} \times \frac{1}{\frac{1}{R_1} + \frac{1}{5000} + \frac{1}{4000}}$$

$$\frac{1}{1300} = \frac{1}{R_1} + \frac{1}{5000} + \frac{1}{4000}$$

$$\frac{1}{R_1} = \frac{1}{1300} - \frac{1}{5000} - \frac{1}{4000}$$

$$R_1 = 3.1 \text{ k}\Omega$$