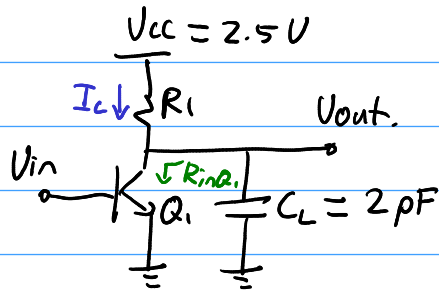


11.1



-3dB bandwidth: 1 GHz.

Power budget = 2 mW.

(bias network not shown).

From the power budget,  $I_C = \frac{P}{V_{CC}} = \frac{0.002}{2.5} = 0.8 \text{ mA}$ .


$\therefore g_m = \frac{I_C}{V_T} = \frac{0.8}{26} = 30.77 \text{ mS}$ .

Gain at DC =  $-g_m R_i$

Since  $V_A = \infty$ , transistor  $r_o = \infty$  and it acts like a current source.  $\therefore R_{in, Q1} = \infty$ .

$\therefore$  The pole at  $V_{out}$  sees only  $R_i$  to AC ground.

$$\omega_p = \frac{1}{R_i C_L}$$

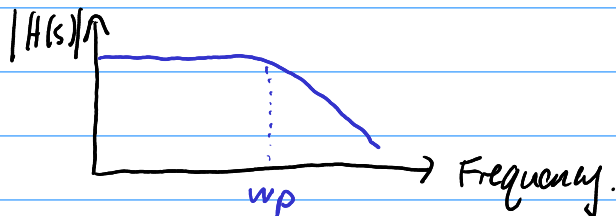

We want  $f_p = 1 \text{ GHz}$

$$\therefore 1 \times 10^9 = \frac{1}{2\pi R_i \times 2 \times 10^{-12}}$$

$$R_i = 79.58 \Omega.$$

This the max value to meet the bandwidth.

$\therefore$  DC gain =  $-g_m R_i = -2.45$ .