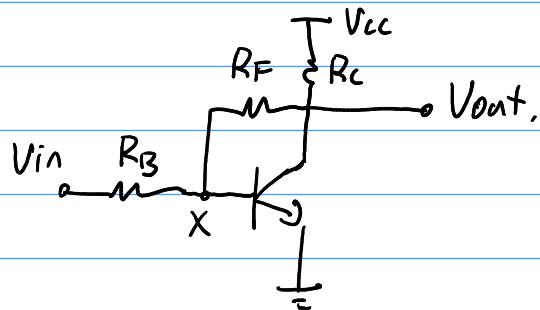



11.16



Assume $V_A = \infty$

$$R_F \text{ large} \therefore \frac{V_{out}}{V_x} = -g_m R_C.$$

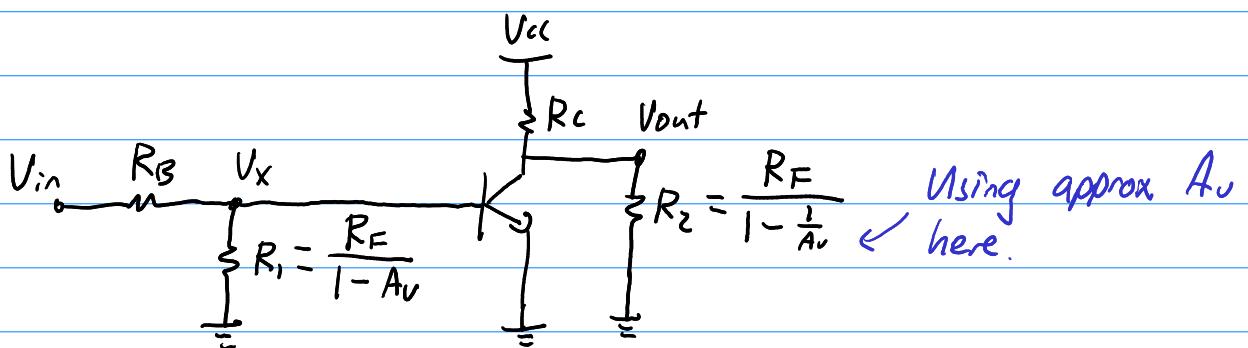Transform this circuit using Miller's Theorem.



Impedances are divided by $(1 - A_v)$ & $(1 - \frac{1}{A_v})$ respectively.

$$R_1 = \frac{R_F}{1 + g_m R_C}, \quad R_2 = \frac{R_F}{1 + \frac{1}{g_m R_C}} \approx R_F. \quad \text{Also } R_F \gg R_C.$$

Notice voltage divider at $V_x = \frac{V_{in} R_1}{R_B + R_1}$

$$\begin{aligned} \therefore \frac{V_{out}}{V_{in}} &= \frac{V_{out}}{V_x} \frac{V_x}{V_{in}} = -g_m R_C \frac{R_1}{R_B + R_1} \\ &= -\frac{-g_m R_C \frac{R_F}{1 + g_m R_C}}{R_B + \frac{R_F}{1 + g_m R_C}} = \frac{-g_m R_C R_F}{R_B (1 + g_m R_C) + R_F} \\ &= \frac{-g_m R_C}{1 + K} \xrightarrow{\text{gain without } R_F} \text{gain reduction in gain.} \end{aligned}$$

$$\text{where } K = \frac{R_B}{R_F} (1 + g_m R_C)$$