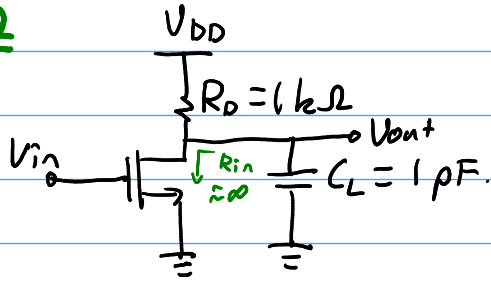


11.2



Find f at which
gain falls by 10%.
Bias network not shown.

$$\text{DC gain} = -g_m R_D = -1000g_m.$$

$$\text{One pole at } \omega_p = \frac{1}{R_D C_L} = \frac{1}{1000C_L}$$

$$\therefore \text{Transfer function is } H(s) = \frac{-1000g_m}{1 + \frac{s}{\omega_p}} = \frac{-1000g_m}{1 + 1000sC_L}$$

Note: could also have found this by circuit analysis.

$$\begin{aligned} H(s) &= \frac{V_{out}}{V_{in}} = -g_m \left(R_D \parallel \frac{1}{sC_L} \right) = -g_m \frac{\frac{R_D}{sC_L}}{R_D + \frac{1}{sC_L}} \\ &= \frac{-g_m R_D}{sR_D C_L + 1} = \frac{-1000g_m}{1 + 1000sC_L} \end{aligned}$$

However finding poles by inspection leads to insight!
It is better to think than do algebra.

$$\text{Want } \left| \frac{H(j\omega)}{H(0)} \right| = 0.9$$

$$\left| \frac{1}{1 + j\omega 1000C_L} \right| = 0.9$$

$$1.1111 = \sqrt{1^2 + (1000\omega C_L)^2}$$

$$1.2346 = 1 + \omega^2 (1000C_L)^2$$

$$(C_L = 1pF)$$

$$\omega = 4.84 \times 10^8 \text{ rad/s}$$

$$f = \frac{\omega}{2\pi} = 77 \text{ MHz.}$$