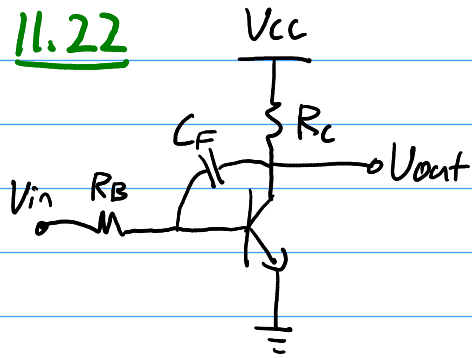


11.22




$$V_A = \infty$$

Find the poles.

Notice $A_v = -g_m R_c$.

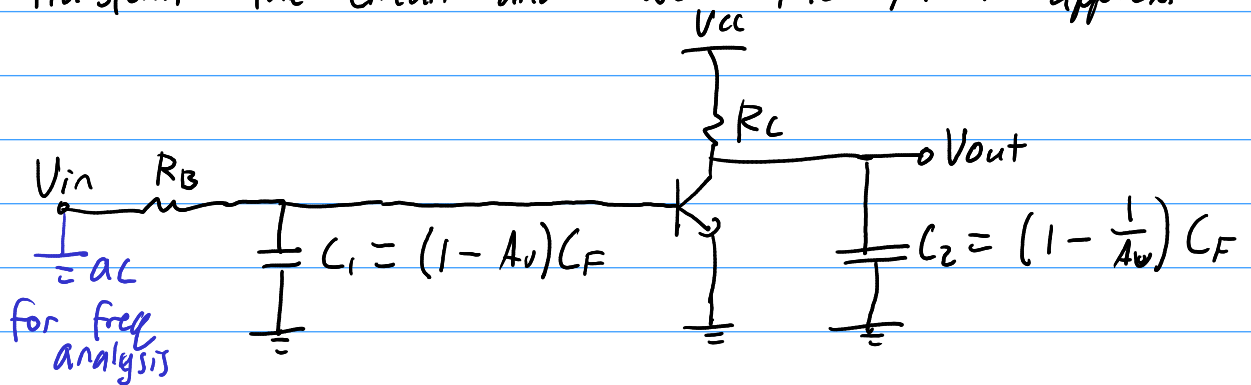Transform the circuit and use the Miller approximation:



$$\text{Input pole: } \omega_1 = \frac{1}{R_B C_1} = \frac{1}{R_B C_F (1 + g_m R_c)}$$

large C \Rightarrow Low freq pole.

$$\text{Output pole: } \omega_2 = \frac{1}{R_c C_2} = \frac{1}{R_c C_F (1 + \frac{1}{g_m R_c})}$$

Smaller multiplication

For reasonable component values, ω_1 is probably the dominant pole (i.e. at lower frequencies).

Having 2 poles is an artefact of the Miller approx, so neglect ω_2 .