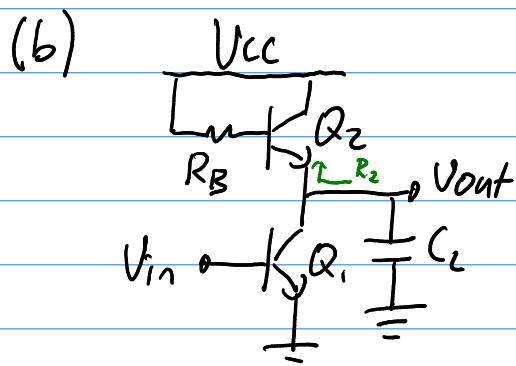


Looking into Q_2 emitter,
 $R_{out} = \frac{1}{g_m 2}$


Looking into Q_1 collector,
 $R_{out} = \infty$ because $V_A = \infty$.

\therefore Only one pole, the -3dB point is $f = \frac{1}{g_m 2 C_L} - \frac{g_m 2}{C_L}$.



Need to find the impedance seen looking into Q_2 's emitter.

Consider small signal model.

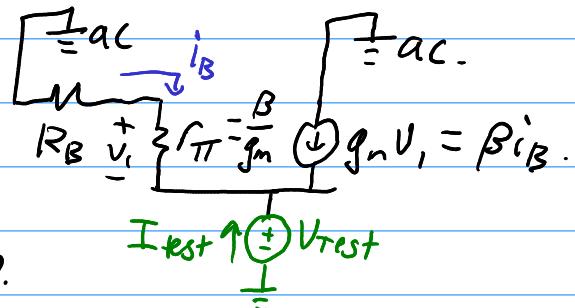

By KCL, $i_B + I_{test} + \beta i_B = 0$

$$\therefore (1 + \beta) i_B + I_{test} = 0.$$


By Ohm's law, $i_B = \frac{0 - V_{test}}{R_B + r_\pi}$

$$\therefore (1 + \beta) \left(\frac{-V_{test}}{R_B + r_\pi} \right) + I_{test} = 0.$$

$$(1 + \beta) V_{test} = (R_B + r_\pi) I_{test} = \left(R_B + \frac{\beta}{g_m} \right) I_{test}$$

$$\frac{V_{test}}{I_{test}} = \frac{R_B + \frac{\beta}{g_m}}{1 + \beta} \approx \frac{R_B + \frac{\beta}{g_m}}{\beta} = \frac{1}{g_m} + \frac{R_B}{\beta}.$$

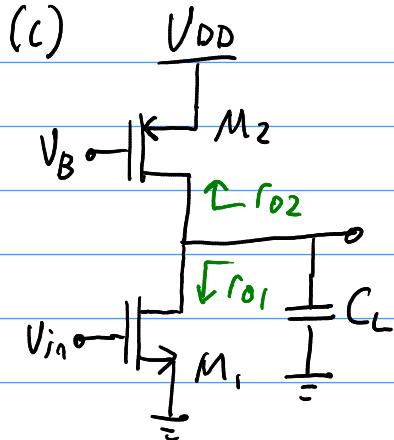
$$\therefore -3\text{dB} \text{ point is } \frac{1}{2\pi C_L \left(\frac{1}{g_m} + \frac{R_B}{\beta} \right)}$$



Notice M_2 is PMOS
 \therefore we are looking into
the drain of both devices.


\therefore Resistances are the r_o of
each transistor.

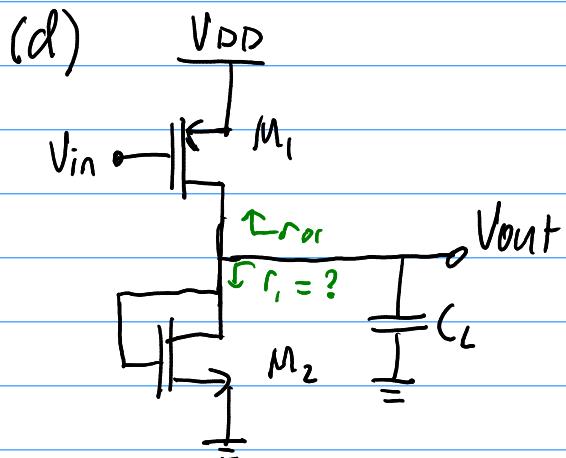$\therefore -3 \text{ dB point is } \frac{1}{2\pi(r_{o1} \parallel r_{o2}) C_L}$



- See r_{o1} looking into M_1 .
- Looking into M_2 , notice that $V_{out} = V_{as}$

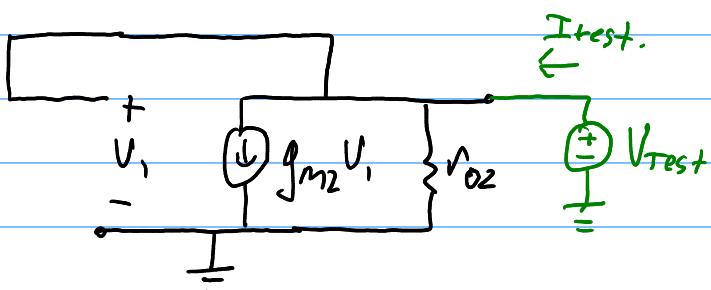\therefore Current is controlled.
Need to check small signal model.



$$V_i = V_{TEST}$$

By KCL: $I_{TEST} = g_m V_{TEST} + \frac{V_{TEST}}{r_{o1}} = (g_m + \frac{1}{r_{o1}}) V_{TEST}$

$$\frac{V_{TEST}}{I_{TEST}} = \frac{1}{g_m + \frac{1}{r_{o1}}} = \frac{1}{g_m} \parallel r_{o1}.$$

$\therefore -3 \text{ dB point is } \frac{1}{2\pi C_L (\frac{1}{g_m} \parallel r_{o1} \parallel r_{o2})}$