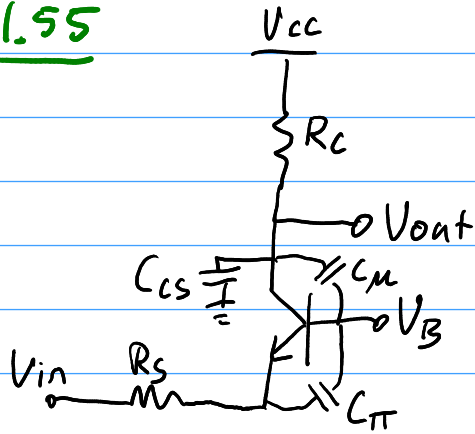


11.55



Design for -3dB bandwidth of 10 GHz , given:

$$I_C = 1\text{ mA}$$

$$V_A = \infty$$

$$R_S = 50\ \Omega$$

$$C_{\pi} = 20\text{ fF}$$

$$C_{\mu} = 5\text{ fF}$$

$$C_{cs} = 20\text{ fF}$$

Find max R_C and hence max gain.

Notice: no caps between V_{in} & V_{out}

\therefore no Miller multiplication.

Consider all independent sources (V_{in} , V_B , V_{cc}) as AC ground.

$$\text{Input pole: } f = \frac{1}{2\pi R_S C_{\pi}} = \frac{1}{2\pi \times 50 \times 20 \times 10^{-15}} \\ = 159\text{ GHz}$$

Very fast, no issue.

$$\text{Output pole: } f = \frac{1}{2\pi R_C (C_{cs} + C_{\mu})} \quad \leftarrow \text{caps in parallel.}$$


$$R_C = \frac{1}{2\pi f (C_{cs} + C_{\mu})} \\ = \frac{1}{2\pi \times 10 \times 10^9 \times (20 + 5) \times 10^{-15}} \\ = 637\ \Omega.$$

To find the max gain, we need to consider the gain equation for this topology.

If R_s were 0 then the gain of the common base core would be $A_v = g_m R_c$.

Where $g_m = \frac{I_c}{V_T} = \frac{1 \text{ mA}}{26 \text{ mV}} = \frac{1}{26} \text{ S}$.

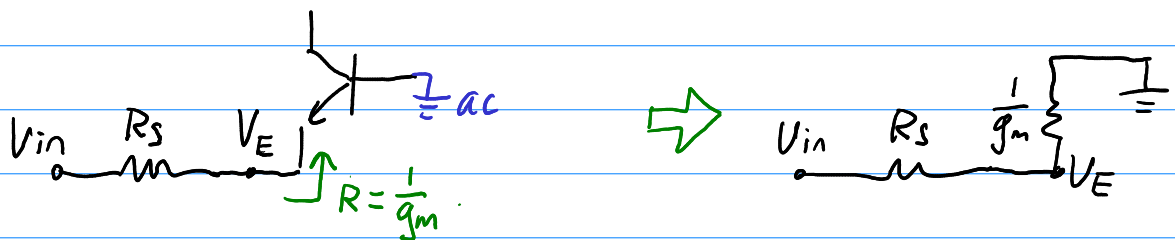Consider that R_s forms a voltage divider with the impedance looking into the emitter.



$$\therefore V_E = \frac{1/g_m}{R_s + 1/g_m} \cdot V_{in}$$

Multiply by the gain of the CB amplifier.

$$\frac{V_{out}}{V_{in}} = \frac{V_{out}}{V_E} \frac{V_E}{V_{in}} = g_m R_c \cdot \frac{1/g_m}{R_s + 1/g_m}$$

$$= \frac{R_c}{R_s + \frac{1}{g_m}}$$

$$= \frac{637}{50 + 26}$$

$$= 8.36$$

← Max gain given bandwidth requirement.