



Common source amp.
with ideal current
source biasing ($R_{in} \rightarrow \infty$)
has only the transistor
 r_o to AC ground.

$$\therefore \text{Open loop DC gain} = -g_m r_o. \quad \text{Big value}$$

There is a pole at V_{out} with $w_p = \frac{1}{r_o C_L}$.

$$\therefore \text{Open loop } H_1(s) = \frac{-g_m r_o}{1 + \frac{s}{w_p}} = \frac{-g_m r_o}{1 + s r_o C_L}$$

$$\text{Low freq loop gain} = -\frac{V_{out}}{V_{test}} = +K g_m r_o.$$

In a feedback network, the bandwidth rises by a factor of $(1 + \text{loop gain})$.

$$\therefore \text{New bandwidth} = (1 + K g_m r_o) \left(\frac{1}{r_o C_L} \right)$$

$$B = \frac{1}{r_o C_L} + \frac{K g_m}{C_L}$$

$$B - \frac{1}{r_o C_L} = \frac{K g_m}{C_L}$$

$$\frac{B C_L}{g_m} - \frac{1}{r_o g_m} = K.$$