
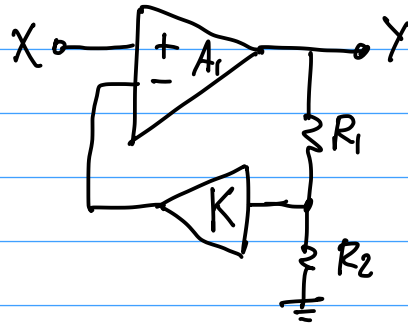


(a)

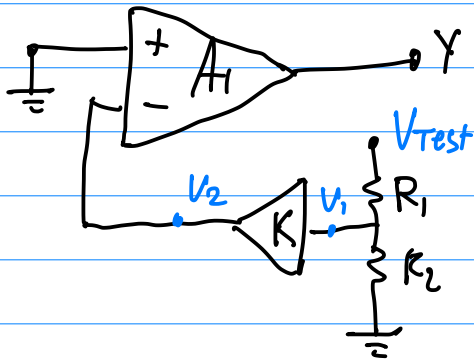

Open loop gain =  $A_1$

For loop gain, set  $X=0$  and break the loop.



$$V_1 = \frac{R_2}{R_1 + R_2} V_{test}$$


$$V_2 = K V_1 = K \frac{R_2}{R_1 + R_2} V_{test}$$

$$Y = -A_1 V_2 = -\frac{A_1 K R_2}{R_1 + R_2} V_{test}$$

$$\text{Loop gain} = \frac{-Y}{V_{test}} = \frac{-A_1 K R_2}{R_1 + R_2}$$

$$\therefore \frac{Y}{X} = \frac{A_1}{1 + \left( \frac{A_1 K R_2}{R_1 + R_2} \right)}$$

(b)

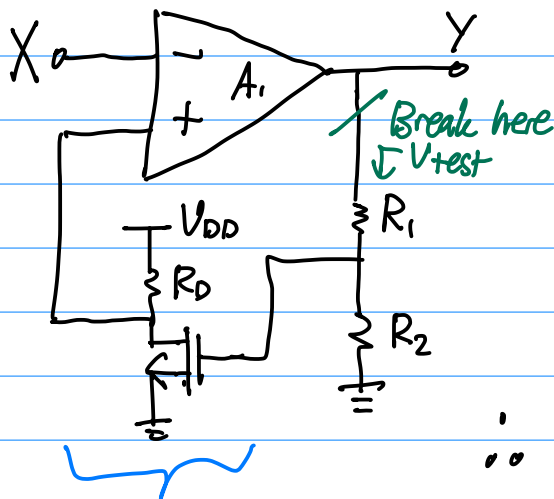

Open loop gain =  $-A_1$


Loop gain =  $\frac{-Y}{V_{test}}$

$$= \frac{+R_2 g_m R_0 A_1}{R_1 + R_2}$$

$$\therefore \frac{Y}{X} = \frac{-A_1}{1 + \left( \frac{A_1 g_m R_0 R_2}{R_1 + R_2} \right)}$$

CS gain =  $-g_m R_0$

(c)

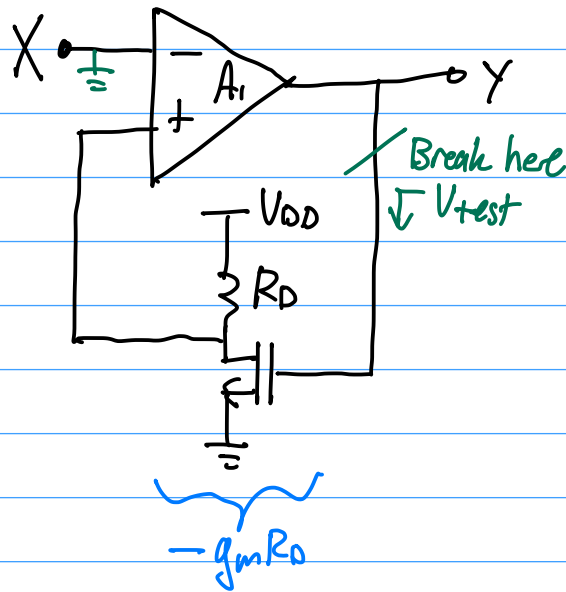


Open loop gain =  $-A_1$

$$\frac{Y}{V_{test}} = -g_m R_D A_1$$

Loop gain =  $+g_m R_D A_1$

$$\therefore \frac{Y}{X} = \frac{-A_1}{1 + g_m R_D A_1}$$

(d)

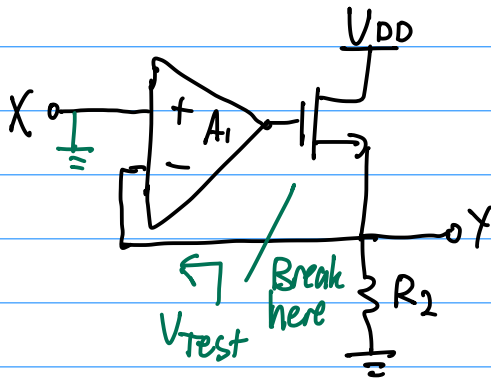

Output is a source follower with gain of

$$\frac{R_2}{\frac{1}{g_m} + R_2}$$

$$\therefore \text{Open loop gain} = \frac{A_1 R_2}{\frac{1}{g_m} + R_2}$$

$$\frac{Y}{V_{test}} = \frac{-A_1 R_2}{\frac{1}{g_m} + R_2}$$

$$\therefore \text{Loop gain} = \frac{+A_1 R_2}{\frac{1}{g_m} + R_2}$$

$$\therefore \frac{Y}{X} = \frac{\left( \frac{A_1 R_2}{\frac{1}{g_m} + R_2} \right)}{1 + \left( \frac{A_1 R_2}{\frac{1}{g_m} + R_2} \right)} \approx 1$$