


$$(a) \quad A_v = \frac{R_L}{R_L + \frac{1}{g_m}}$$

$$\frac{1}{g_m} = \frac{R_L}{A_v} - R_L = \frac{8}{0.8} - 8 = 2 \Omega.$$

$$g_m = 0.5 \text{ S.}$$

$$\therefore I_c = g_m V_T = 0.5 \times 0.026 = 13 \text{ mA.}$$
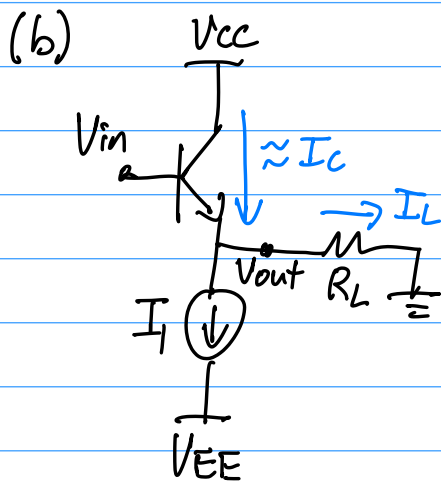
$$\therefore I_1 = I_c = 13 \text{ mA.}$$



Output power of 0.5 W  
corresponds to

$$I_L^2 R_L = 0.5$$

$$I_L^2 = \frac{0.5}{8}$$

$$I_L = 0.25 \text{ A (peak).}$$

At this peak,

$$I_c = I_L - I_1$$

$$= 0.25 - 0.013$$

$$= 0.237 \text{ A.}$$

$$\therefore g_m = \frac{I_c}{V_T} = 9.1 \text{ S.}$$

$$\therefore A_v = \frac{R_L}{R_L + \frac{1}{g_m}} = 0.987.$$

The voltage gain rose from 0.8 to 0.99  
 $\Rightarrow$  non-linear response.