

$$I_C = I_{S1} e^{\frac{V_{BE}}{V_T}}$$

$$I_C = I_L + I_I$$


$$I_L = \frac{V_{out}}{R_L}$$

$$\therefore \frac{V_{out}}{R_L} + I_I = I_{S1} \exp\left(\frac{V_{in} - V_{out}}{V_T}\right)$$

Solve numerically using the symbolic toolbox in Matlab.

When $V_{in} = 1 V$, $V_{out} = 0.113 V$, $V_{BE} = 0.887 V$

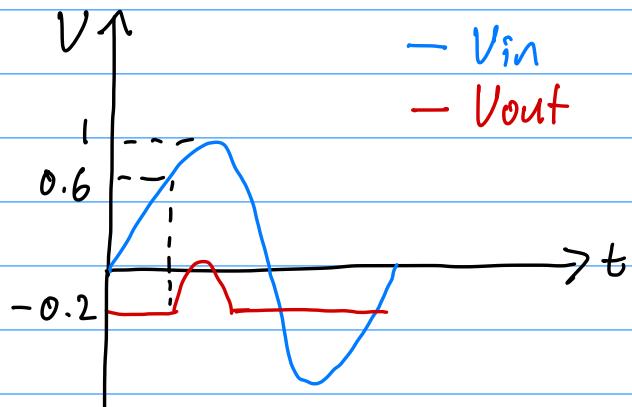When $V_{in} = -1 V$, $V_{out} = -0.2 V$, $V_{BE} = -0.8 V$.



This small integrated transistor has $V_{BE} \approx 0.8 V$
 \therefore Turn on is when
 $V_{in} \approx -0.2 + 0.8 = 0.6 V$.