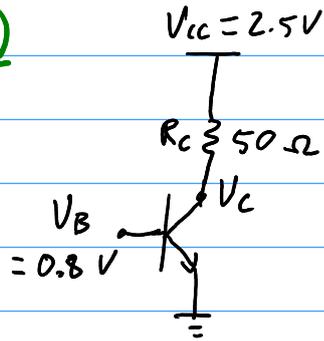


4.21 (a)



If in active region:

$$\begin{aligned} I_c &= I_s e^{V_B/V_T} \\ &= 8 \times 10^{-16} e^{0.8/0.026} \\ &= 18.45 \text{ mA} \end{aligned}$$

check if  $V_c$  is high enough.

$$V_c = 2.5 - I_c R_c = 2.5 - 0.01845 \times 50 = 1.578 \text{ V}.$$


We have  $V_c > V_B > V_E$   $\therefore$  in forward active region.

Calc. parameters for small signal model.

$$g_m = \frac{I_c}{V_T} = \frac{18.45 \text{ mA}}{26 \text{ mV}} = 0.7096 \text{ S}.$$


$$r_{\pi} = \frac{\beta}{g_m} = \frac{100}{0.7096} = 140.9 \text{ } \Omega.$$

$\therefore$  Small signal model is:

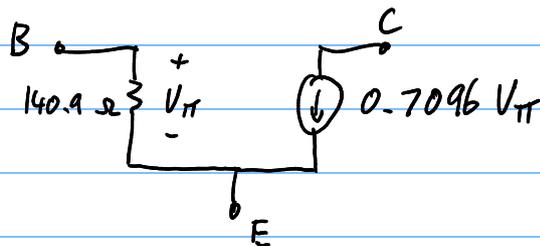

No  $r_o$  since  $V_A = \infty$ .

4.21 (b)

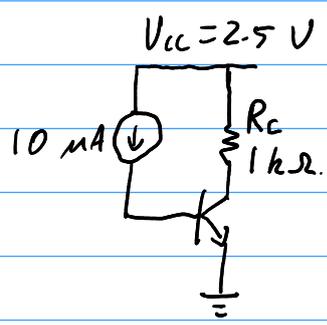


Given  $\beta = 100$   
 $I_s = 8 \times 10^{-16} \text{ A}$   
 $V_A = \infty$


$$I_c = \beta I_b = 100 \times 10 \times 10^{-6} = 1 \text{ mA.}$$

Calc. parameters.  $g_m = \frac{I_c}{V_T} = \frac{1 \times 10^{-3}}{0.026} = 38.46 \text{ mS.}$   
 $r_{\pi} = \frac{\beta}{g_m} = \frac{100}{38.46 \times 10^{-3}} = 2.6 \text{ k}\Omega.$

$\therefore$  Small signal model is:

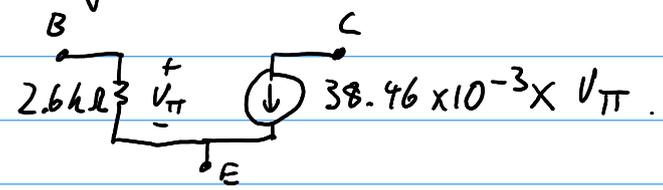

4.21 (c)

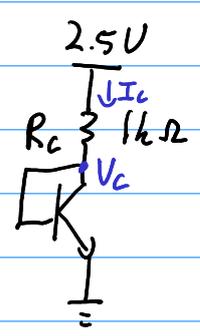

$$V_{BE} = V_B = V_C$$

$$V_C = 2.5 - 1000 I_c$$

$$I_c = I_s e^{V_{BE}/V_T}$$

$$= I_s e^{(2.5 - 1000 I_c)/V_T}$$

Solving numerically (or trial and error)  
 Starting from an initial guess  $V_{BE} \approx 0.7 \text{ V.}$   
 $\Rightarrow I_c = 1.76 \text{ mA.}$

$\therefore g_m = \frac{I_c}{V_T} = 67.7 \text{ mS.}$   
 $r_{\pi} = \frac{\beta}{g_m} = 1.48 \text{ k}\Omega.$

