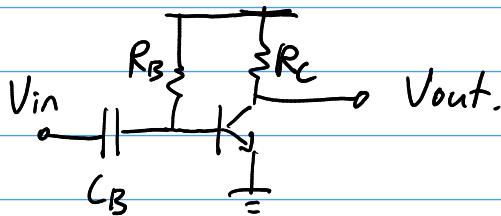


5.74


Given $\beta = 100$, $I_S = 6 \times 10^{-16} A$, $V_A = \infty$

Design a common emitter for $|Av| = 10$,
 $R_{in} > 5 k\Omega$, $R_{out} = 1 k\Omega$.

$$V_{CC} = 2.5 V$$



Draw the small signal model

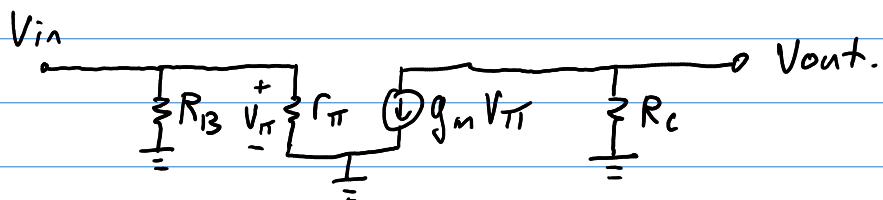

Notice $R_{out} = R_C \therefore R_C = 1 k\Omega$.

Now find the required bias point.

$$|Av| = g_m R_C = 1000 g_m = 10.$$

$$\therefore g_m = 10 \text{ mS.}$$

$$I_C = g_m V_T = 10 \times 10^{-3} \times 26 \times 10^{-3}$$
$$= 260 \mu A.$$

$$\therefore I_B = \frac{I_C}{\beta} = 2.6 \mu A.$$

Using KVL from V_{CC} through R_B to ground:


$$V_{CC} = I_B R_B + V_{BE} \quad (1)$$

$$\text{Also, } V_{BE} = V_T \ln \left(\frac{I_C}{I_S} \right) = 0.026 \times \ln \left(\frac{260 \times 10^{-6}}{6 \times 10^{-16}} \right)$$
$$= 696.7 \text{ mV.}$$

$$\therefore \text{From (1), } 2.5 = 2.6 \times 10^{-6} \times R_B + 0.6967$$
$$R_B = 694 \text{ k}\Omega.$$

$$\text{Check } R_{in} = R_B \parallel r_\pi = R_B \parallel \left(\frac{\beta}{g_m} \right) = 9.86 \text{ k}\Omega > 5 \text{ k}\Omega \checkmark$$

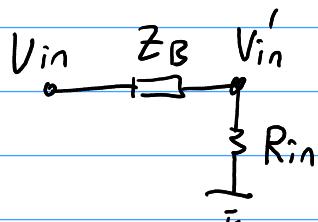To size C_B , notice that it forms an AC voltage divider with R_{in} .



A plausible design choice is for $|Z_B| = 0.1 R_{in}$.

$$\therefore \frac{1}{\omega C_B} = 0.1 R_{in}$$

$$\omega = 2\pi \times 200 = 400\pi$$

$$\therefore \frac{1}{400\pi C_B} = 0.1 \times 9.86 \times 10^3$$

$$C_B(\text{min}) \approx 800 \text{ nF.}$$