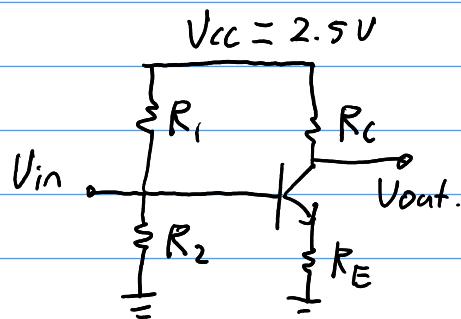


5.80




Design CE for: gain = 5

$$R_{out} = 500 \Omega.$$

Assume R_E voltage drop = 0.3 V.

Current in $R_1 \approx 10 I_B$.

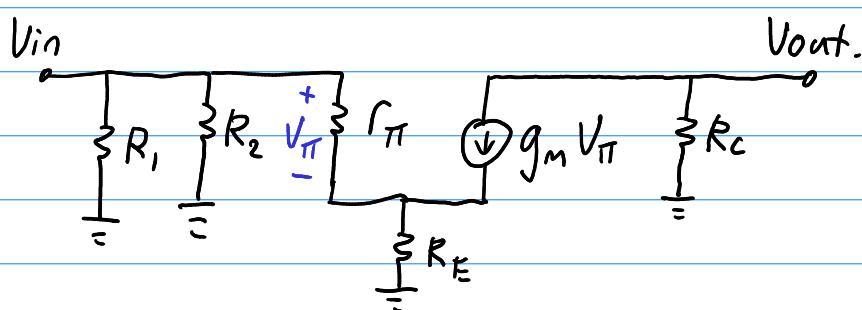Draw small signal model. $f_0 = \infty \because V_A = \infty$.



Output impedance is defined with $V_{in} = 0 \therefore V_{pi} = 0$

\therefore Current source is open circuit $\therefore R_{out} = R_C$

\therefore By the design spec, $R_{out} = 500 \Omega \therefore R_C = 500 \Omega$.

R_E voltage drop $\approx 0.3 V \therefore I_E R_E = 0.3$

$$\therefore R_E = \frac{0.3}{I_E} \approx \frac{0.3}{I_C}.$$

Gain of degenerated CE = $\frac{-R_C}{1/g_m + R_E}$

(By circuit analysis,
see lecture notes).

$$\text{Also } g_m = \frac{I_C}{V_T}$$

$$\therefore S = \frac{500}{\frac{0.026}{I_C} + \frac{0.3}{I_C}} = \frac{500 I_C}{0.026 + 0.3}$$

$$\therefore I_C = 3.26 \text{ mA.}$$


$$\therefore R_E = \frac{0.3}{I_C} = 92 \Omega.$$

Now design the bias network.

$$V_{BE} = V_T \ln \left(\frac{I_C}{I_S} \right) = 0.026 \ln \left(\frac{3.26 \times 10^{-3}}{6 \times 10^{-16}} \right) \\ = 0.7624 \text{ V.}$$

$$V_B = V_{BE} + V_E = 0.7624 + 0.3 = 1.0624 \text{ V.}$$

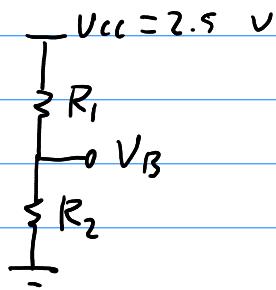Neglecting I_B , we have a simple voltage divider.



$$V_B = \frac{V_{CC} R_2}{R_1 + R_2}$$

$$1.0624 (R_1 + R_2) = 2.5 R_2. \quad (1)$$


The spec says $I(R_1) = 10 I_B = 10 \frac{I_C}{\beta} = 326 \mu\text{A}$.

$$\therefore R_1 = \frac{2.5 - 1.0624}{326 \times 10^{-6}} = 4.41 \text{ k}\Omega.$$

$$\text{From (1)} : 1.0624 (4.41 \text{ k}\Omega + R_2) = 2.5 R_2 \\ R_2 = 3.26 \text{ k}\Omega.$$

Check for active region.
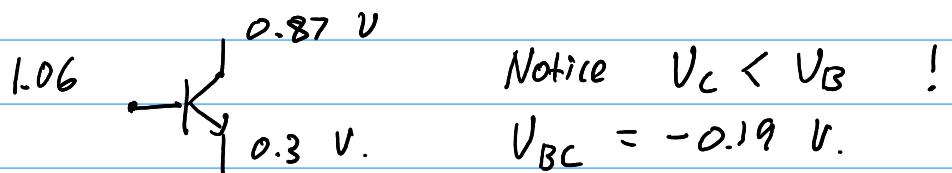
$$V_C = 2.5 - I_C R_C = 2.5 - 3.26 \times 10^{-3} \times 500 = 0.87 \text{ V.}$$



\therefore In soft saturation ... this is OK but not ideal.