
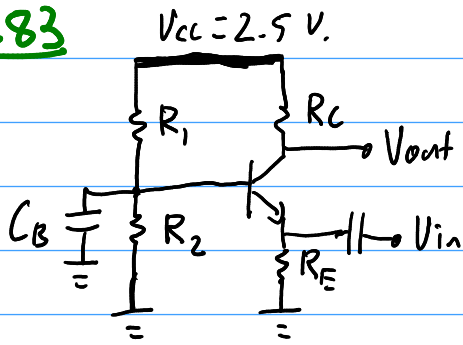


5.83

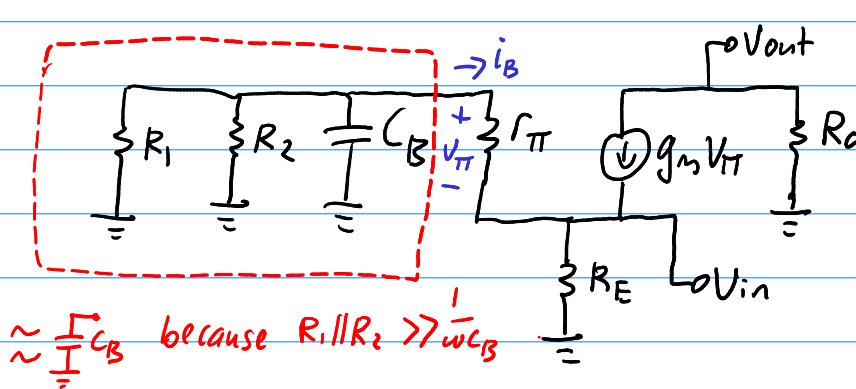

Design a common base stage for voltage gain of 20, $R_{in} = 50 \Omega$.
 $V(R_E) = 260 \text{ mV}$.
 $I(R_1) = 10 I_B$
 $f_{min} = 200 \text{ Hz}$.


Small signal model:



$$r_{\pi} = \frac{\beta}{g_m}$$

$$g_m = \frac{I_C}{V_T}$$

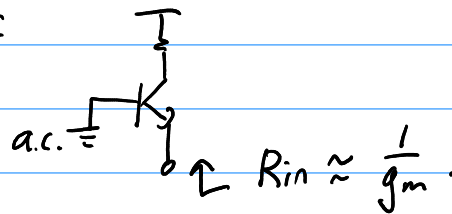Since C_B will have a low impedance to AC, we can use the rule:



Also $R_E \gg \frac{1}{g_m}$
 $\therefore R_E || \frac{1}{g_m} \approx \frac{1}{g_m}$

$$\therefore R_{in} = 50 = \frac{1}{g_m} \quad \therefore g_m = \frac{1}{50} \text{ S}$$

$$\therefore I_C = g_m V_T = \frac{1}{50} \times 0.026 = 520 \mu\text{A}$$

Since we want $V(R_E) \approx 0.26$, $R_E \approx \frac{0.26}{I_C} = 500 \Omega$.

From the small signal model, V_{π} is a voltage divider:

$$V_{\pi} = \frac{-V_{in} r_{\pi}}{r_{\pi} + Z_B} = \frac{-V_{in} \frac{\beta}{g_m}}{\frac{\beta}{g_m} + Z_B} = \frac{-V_{in} \frac{1}{g_m}}{\frac{1}{g_m} + \frac{Z_B}{\beta}}$$

$$\therefore V_{out} = -g_m V_{\pi} R_C = \frac{+V_{in} R_C}{\frac{1}{g_m} + \frac{Z_B}{\beta}}$$

$$\therefore \text{Gain is } \frac{V_{out}}{V_{in}} = \frac{R_c}{\frac{1}{g_m} + \frac{Z_B}{\beta}} \approx g_m R_c$$

$$\text{where we choose } \left| \frac{Z_B}{\beta} \right| \ll \frac{1}{g_m}$$

Since the required gain is 20:

$$20 = g_m R_c = \frac{1}{50} \cdot R_c \Rightarrow R_c = 1 \text{ k}\Omega$$

$$\text{Next choose } C_B. \quad \left| \frac{Z_B}{\beta} \right| = \frac{1}{10} \cdot \frac{1}{g_m}$$

$$\text{Using } f = 200 \text{ Hz:} \quad \frac{1}{2\pi \times 200 C_B \times 100} = \frac{1}{10} \cdot 50$$

$$C_B = 1.59 \mu\text{F}$$

$$\text{Now design the biasing. } V_{BE} = V_T \ln\left(\frac{I_C}{I_S}\right)$$


$$= 0.7147 \text{ V}$$

$$\therefore V_B = V_{BE} + V(R_E) = 0.7147 + 0.26 = 0.9747 \text{ V}$$

$$I(R_1) = 10 I_B = 10 \cdot \frac{I_C}{\beta} = 52 \mu\text{A}$$

$$\therefore R_1 = \frac{2.5 - 0.9747}{52 \times 10^{-6}} = 29.3 \text{ k}\Omega$$
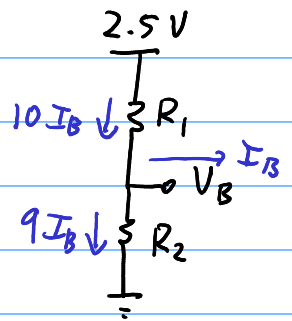
$$\text{Also } R_2 = \frac{V_B}{9 I_B} = \frac{0.9747}{9 \times I_C / \beta} = 20.8 \text{ k}\Omega$$



$$\text{Check for active region. } V_C = 2.5 - I_C R_c = 1.98 \text{ V}$$

