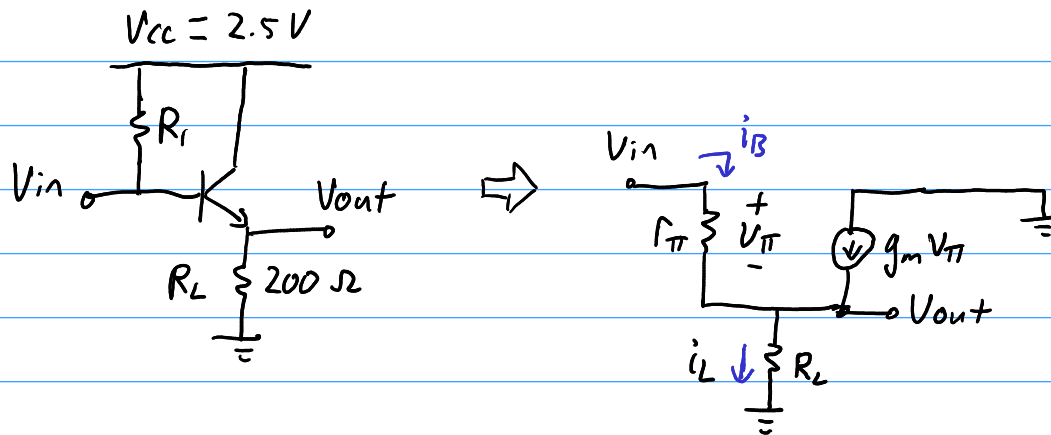


5.88

Design emitter follower for $A_v = 0.85$,
 $R_{in} > 10 \text{ k}\Omega$, $R_L = 200 \Omega$.



By KCL at V_{out} : $i_L = i_B + g_m V_{\pi}$

$$\frac{V_{out}}{R_L} = \frac{V_{\pi}}{r_{\pi}} + g_m V_{\pi} = \left(\frac{1}{r_{\pi}} + g_m \right) V_{\pi}$$

$$\therefore V_{\pi} = \frac{1}{\frac{1}{r_{\pi}} + g_m} \times \frac{V_{out}}{R_L}$$

Since $r_{\pi} = \frac{\beta}{g_m}$, $\frac{1}{r_{\pi}} = \frac{g_m}{\beta}$ $\therefore g_m \gg \frac{1}{r_{\pi}}$

$$\therefore V_{\pi} \approx \frac{V_{out}}{g_m R_L}$$

By KVL from V_{in} to ground: $V_{in} = V_{\pi} + V_{out}$.

$$\therefore V_{in} = \frac{V_{out}}{g_m R_L} + V_{out} = \left(\frac{1 + g_m R_L}{g_m R_L} \right) V_{out}$$

$$\frac{V_{out}}{V_{in}} = A_v = \frac{g_m R_L}{1 + g_m R_L}$$

Given $A_v = 0.85$ and $R_L = 200 \Omega$,

$$0.85 (1 + 200 g_m) = 200 g_m$$

$$0.85 = (200 - 0.85 \times 200) g_m$$

$$g_m = 28.33 \text{ mS}$$

$$\therefore I_C = V_T g_m = 736.7 \mu\text{A}$$

Design bias (R_1). $V_{BE} = V_T \ln\left(\frac{I_C}{I_S}\right) = 0.7237 \text{ V}$.


$$V_E = I_E R_L \approx I_C R_L = 0.1473 \text{ V}$$

$$V_B = V_{BE} + V_E = 0.8711 \text{ V}$$


$$R_1 = \frac{V_{CC} - V_B}{I_B}$$

$$= \frac{V_{CC} - V_B}{I_C/\beta}$$

$$= 221.1 \text{ k}\Omega$$

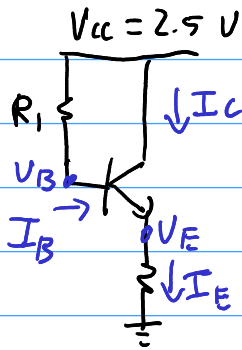

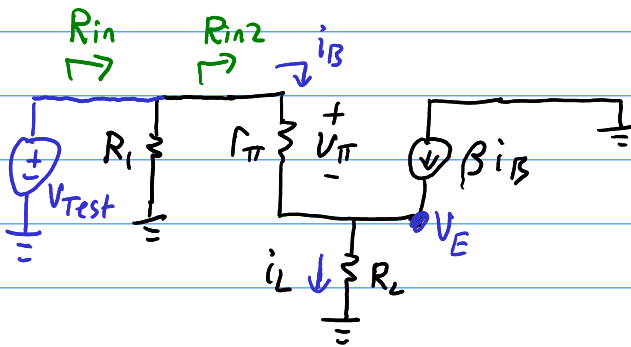Check input resistance $R_{in} > 10 \text{ k}\Omega$.



$$R_{in} = R_1 \parallel R_{in2}$$

To calc. R_{in2} , notice that the impact of R_L is amplified by the current source.

$$V_{test} = i_B r_{\pi} + (i_B + \beta i_B) R_L$$

$$\therefore \frac{V_{test}}{i_B} = R_{in2} = r_{\pi} + (1 + \beta) R_L$$

$$r_{\pi} = \frac{\beta}{g_m} = \frac{100}{28.33 \times 10^{-3}} = 3.53 \text{ k}\Omega$$

$$R_{in2} = 3.53 \times 10^3 + (1 + 100) \times 200 = 23.73 \text{ k}\Omega$$

$$\therefore R_{in} = R_1 \parallel R_{in2} = 221.1 \text{ k}\Omega \parallel 23.73 \text{ k}\Omega = 21.4 \text{ k}\Omega$$

\therefore Exceeds the requirement. \checkmark