
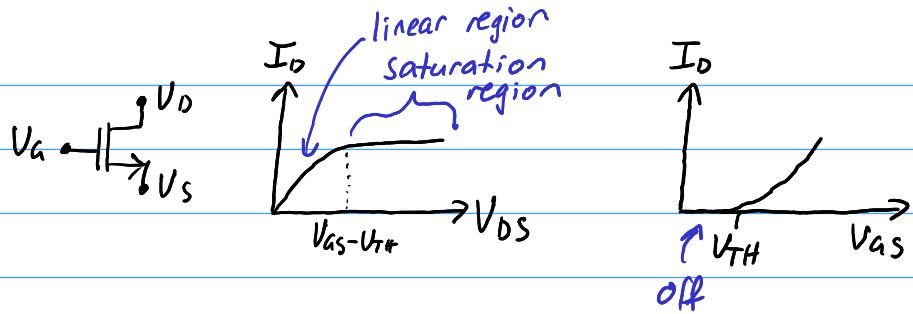


6.20

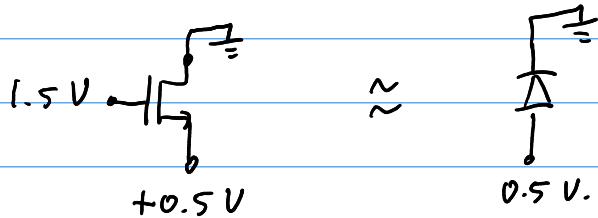

- (a) Transistor is off because \$V_{AS} = 0\$.
- (b) \$V_{AS} = 1\$ V \$\therefore V_{AS} - V_{TH} = 0.6\$ V.
\$V_{DS} = 1.5\$ V. \$V_{DS} > V_{AS} - V_{TH}\$. \$\therefore\$ Saturation region.
- (c) \$V_{DS} = 0 \therefore I_D = 0 \therefore\$ Off.
- (d) Assuming the substrate is shorted to source (as normal) then the body diode is weakly forward biased.



This is not enough for significant conduction.

\$\therefore\$ Neglect body diode effects

\$\therefore\$ Transistor is symmetric w.r.t. source & drain.

Low \$|V_{DS}| \therefore\$ Linear region.

Note: avoid negative \$V_{DS}\$ in general!

- (e) Low \$V_{DS} \therefore\$ Linear.
- (f) All voltages 0 \$\therefore\$ Off.
- (g) \$V_{AS} = 0.5\$ V. \$\therefore V_{AS} - V_{TH} = 0.1\$ V.
\$V_{DS} = 0.5\$ V \$\therefore V_{DS} > V_{AS} - V_{TH} \therefore\$ Saturation.
- (h) Similar to (g) \$\therefore\$ Saturation
- (i) \$V_{AS} = 0.5\$ V \$\therefore V_{AS} - V_{TH} = 0.1\$ V.
\$V_{DS} = 1\$ V \$\therefore V_{DS} > V_{AS} - V_{TH} \therefore\$ Saturation