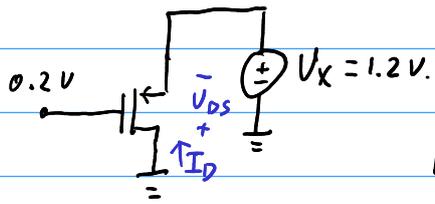


7.15



$$\frac{W}{L} = \frac{10}{0.25}, \quad \lambda = 0.1 \text{ V}^{-1}$$

Notice: PMOS type!  $\mu_p C_{ox} = 100 \times 10^{-6} \frac{\text{A}}{\text{V}^2}$

$$I_D = -\frac{1}{2} \mu_p C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 - \lambda V_{DS})$$

$$V_{GS} = 0.2 - 1.2 = -1 \text{ V}$$


$$V_{DS} = -1.2 \text{ V}$$

$$\begin{aligned} \therefore I_D &= -\frac{1}{2} \times 100 \times 10^{-6} \times \frac{10}{0.25} \times (-1 - (-0.4))^2 (1 - 0.1 \times (-1.2)) \\ &= -0.806 \text{ mA} \end{aligned}$$

In case we aren't sure about  $g_m$  for PMOS, start from first principles.  $g_m = \frac{\partial I_D}{\partial V_{GS}}$ . Include  $\lambda$  this time.

$$\begin{aligned} g_m &= \frac{\partial I_D}{\partial V_{GS}} = -\mu_p C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) (1 - \lambda V_{DS}) \\ &= -100 \times 10^{-6} \times \frac{10}{0.25} \times (-1 - (-0.4)) (1 - 0.1 \times (-1.2)) \\ &= 2.69 \text{ mS} \end{aligned}$$

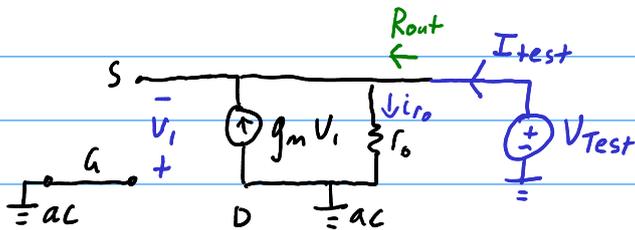Consider the small signal model.  $r_o = \frac{1}{\lambda I_D} = 12.41 \text{ k}\Omega$



Notice  $V_i = -V_{test}$ .

$$\begin{aligned} \text{By KCL at the source: } g_m V_i + I_{test} &= \frac{V_{test}}{r_o} \\ -g_m V_{test} + I_{test} &= \frac{V_{test}}{r_o} \end{aligned}$$

$$I_{test} = \left( \frac{1}{r_o} + g_m \right) V_{test}$$

$$\therefore \frac{V_{test}}{I_{test}} = \frac{1}{\frac{1}{r_o} + g_m}$$

Subst. known values.

$$\frac{V_{test}}{I_{test}} = R_{out} = 360.9 \Omega$$