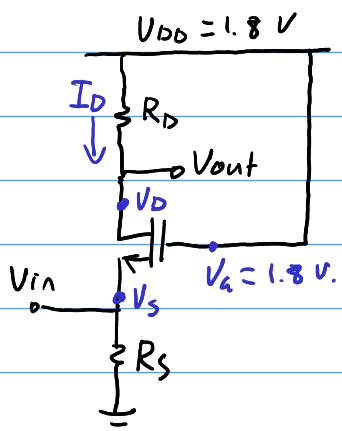


7.68

Design CB amplifier for $A_v = 4$, power budget of 2 mW, and to operate 100 mV away from the triode region.



$$I_D = \frac{P}{V_{DD}} = \frac{0.002}{1.8} = 1.11 \text{ mA.}$$

Analyse the bias point.

V_{DS} is 0.1 V away from triode

$$\therefore V_{DS} = V_{GS} - V_{TH} + 0.1 = V_{GS} - 0.3$$

$$V_{GS} = V_a - V_s = 1.8 - I_D R_s = 1.8 - (1.11 \times 10^{-3}) R_s$$

$$\therefore V_{DS} = 1.8 - (1.11 \times 10^{-3}) R_s - 0.3$$

$$= 1.5 - (1.11 \times 10^{-3}) R_s.$$

$$\text{By KCL, } V_{DD} = I_D R_D + V_{DS} + I_D R_s$$

$$1.8 = (1.11 \times 10^{-3}) (R_D + R_s) + 1.5 - (1.11 \times 10^{-3}) R_s$$

$$0.3 = (1.11 \times 10^{-3}) R_D$$

$$R_D = 270 \Omega.$$

Analyse the required transconductance. $A_v = g_m R_o$

$$\therefore g_m = \frac{A_v}{R_o} = \frac{4}{270} = 14.82 \text{ mS.}$$

This will require a certain V_{GS} .

$$g_m = \frac{2I_D}{V_{GS} - V_{TH}} = 14.82 \times 10^{-3} = \frac{2 \times 1.11 \times 10^{-3}}{V_{GS} - 0.4}$$

$$\therefore V_{GS} = 0.55 \text{ V.}$$

In turn, this requires a certain R_s .

$$V_{GS} = V_a - V_s = 1.8 - I_D R_s$$

$$0.55 = 1.8 - (1.11 \times 10^{-3}) R_s$$

$$R_s = 1.125 \text{ k}\Omega.$$

Find the required $\frac{w}{L}$ from the transistor characteristic:

$$I_D = \frac{1}{2} M_n C_{ox} \frac{w}{L} (V_{GS} - V_{TH})^2$$

$$\frac{w}{L} = 494.$$