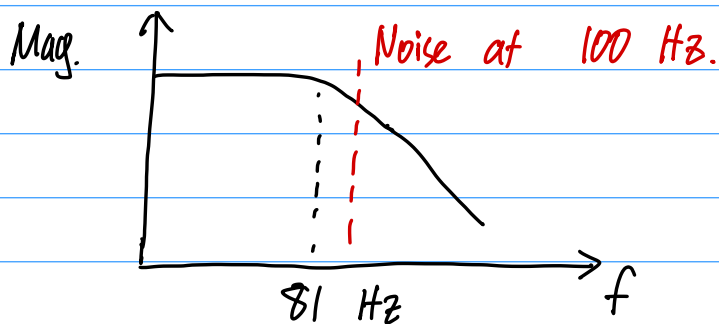


(a) Pole at  $V_{ref}$  with  $R = R_1 \parallel r_o$   
 $= 1000 \parallel 20$   
 $= 19.6 \Omega$   
 $C = 100 \mu F$

$$f_p = \frac{1}{2\pi RC} = 81 \text{ Hz.}$$



(b) Pole with  $R = \frac{R_1}{2} \parallel \left( \frac{R_1}{2} + r_o \right)$   
 $= 519 \Omega$   
 $C = 100 \mu F$

$$f_p = \frac{1}{2\pi RC} = 3 \text{ Hz.}$$

